

creativity & computation lab

week 6 || electrifying!

review

WHERE WE HAVE BEEN

What we have done:

Arrays + OOP

Libraries

GIT

agenda

WHERE WE ARE GOING

What's on for today:

Check out assignments from last class

What IS electricity?!

Voltage, resistance, and current

Ohm's law of course

Breadboards

Field Trip!

Components

Circuits

Parallel v. Series

Switches

Variable Resistors

last assignment

PRESENT


Let's see them libraries!

electricity

SUPER HARD CONCEPT FOR ALL TO GRASP

What is electricity?

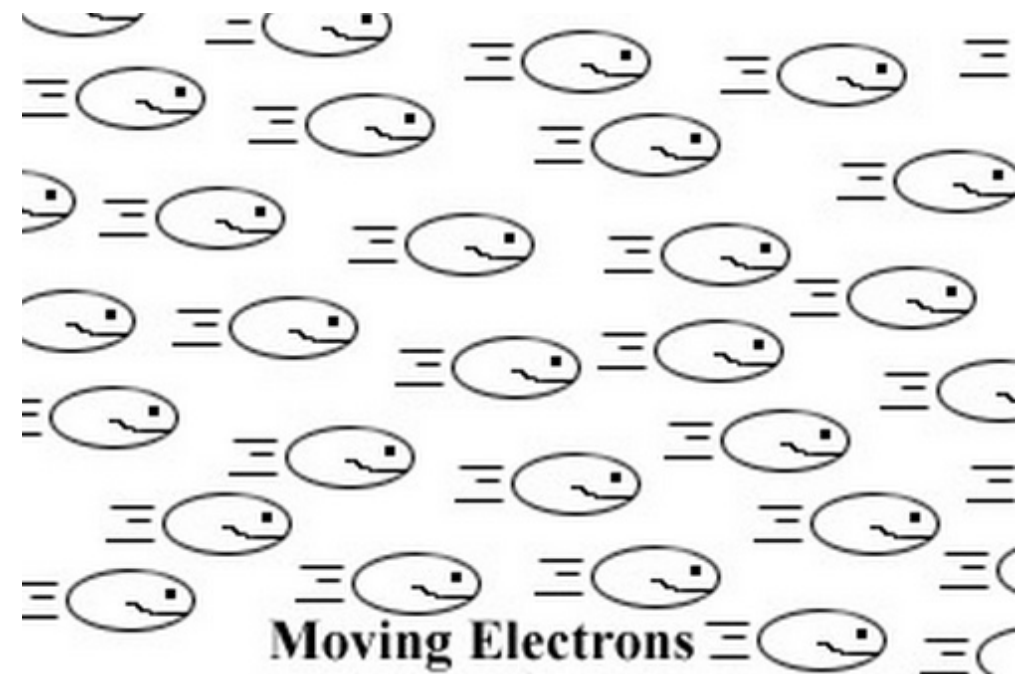Electrical currents are created by a **stream of moving electrons**.




electricity

SUPER HARD CONCEPT FOR ALL TO GRASP


What is electricity?

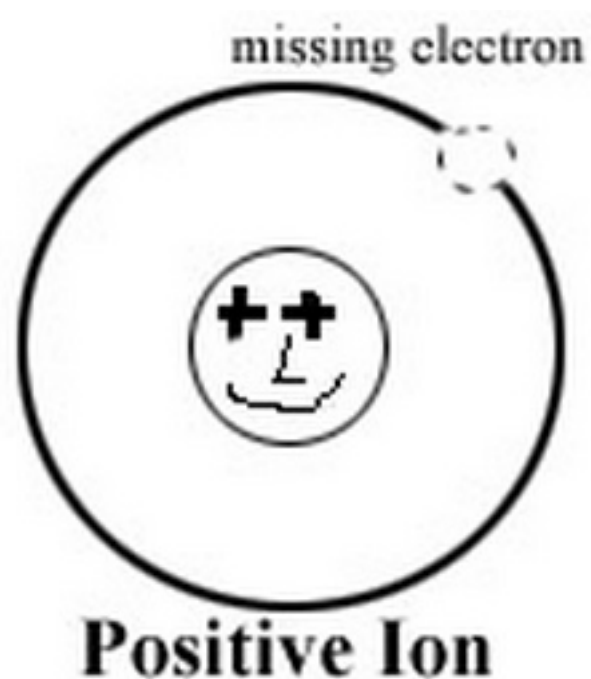The electrons will move when they are attracted by positively charged ions. The electrons (negative charge) **want to fill the voids left by missing electrons.**





electricity

A CONCRETE EXAMPLE ON AN ATOMIC LEVEL

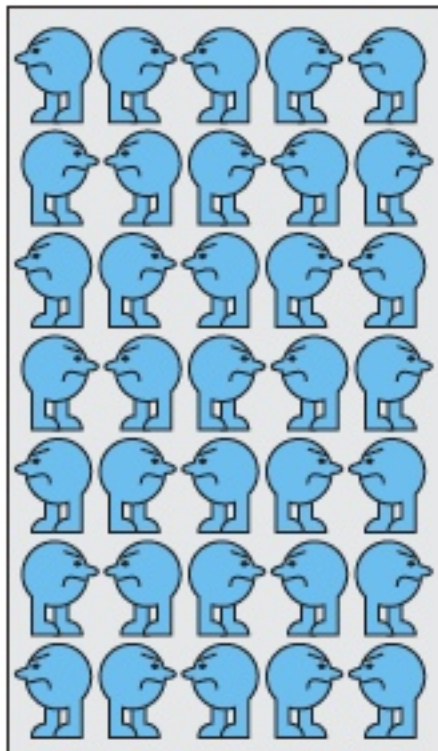

electricity

A CONCRETE EXAMPLE ON AN ATOMIC LEVEL

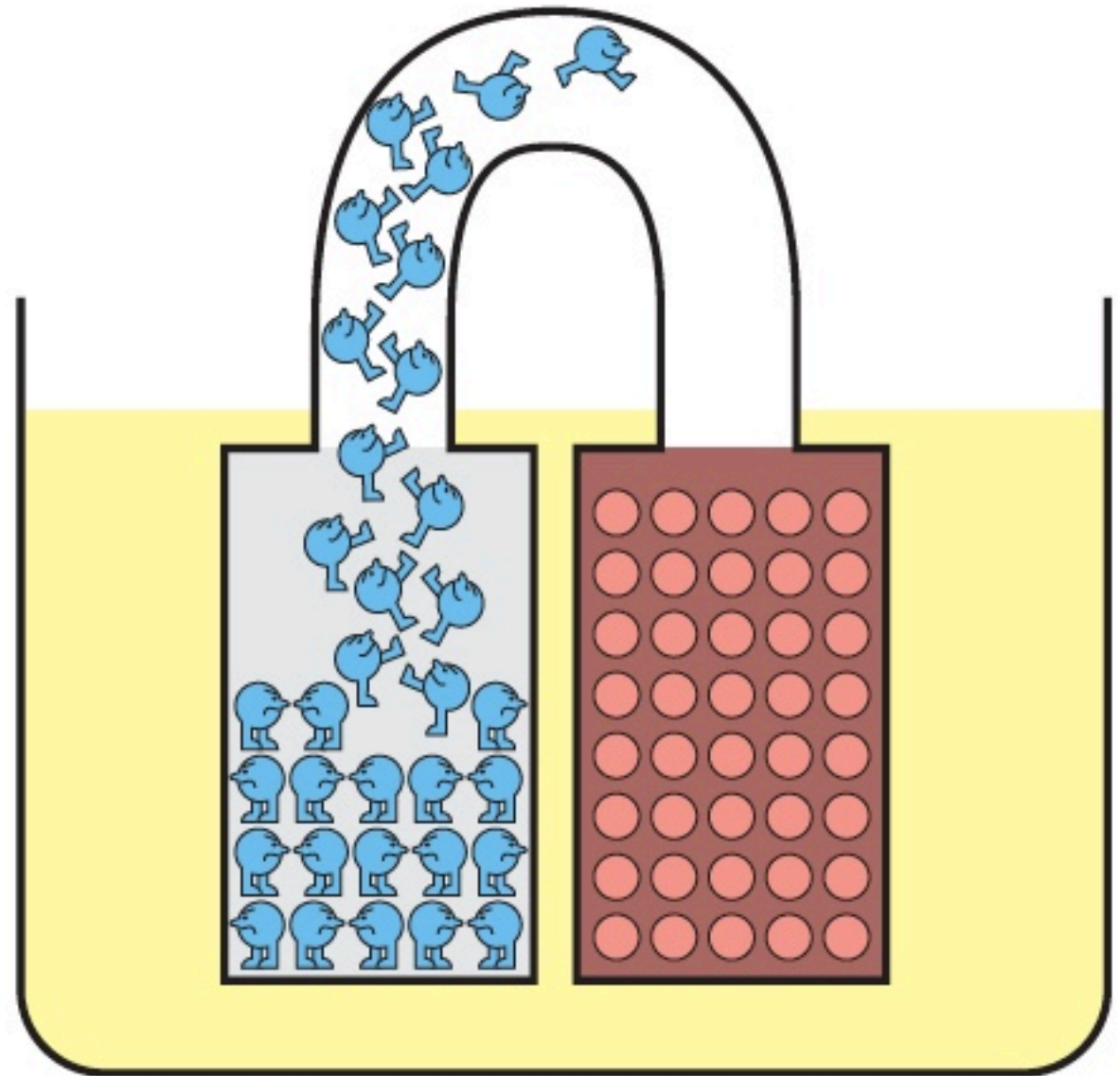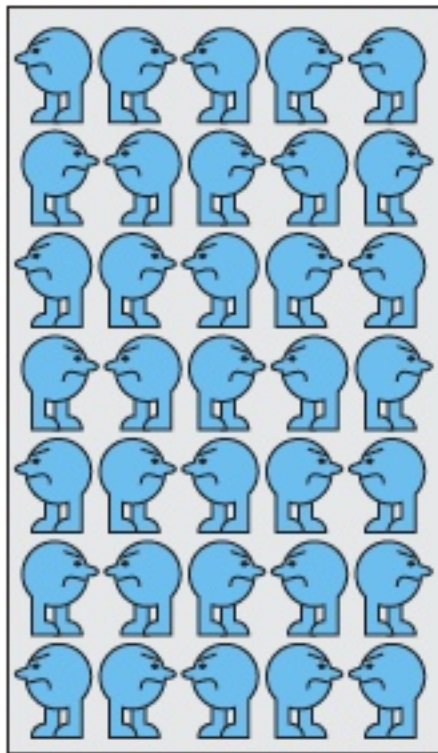


overview: the big three

VOLTAGE, RESISTANCE, AND CURRENT

Power

The work performed by an electrical current.
Measured in Watts.

The dudes with the ladder.

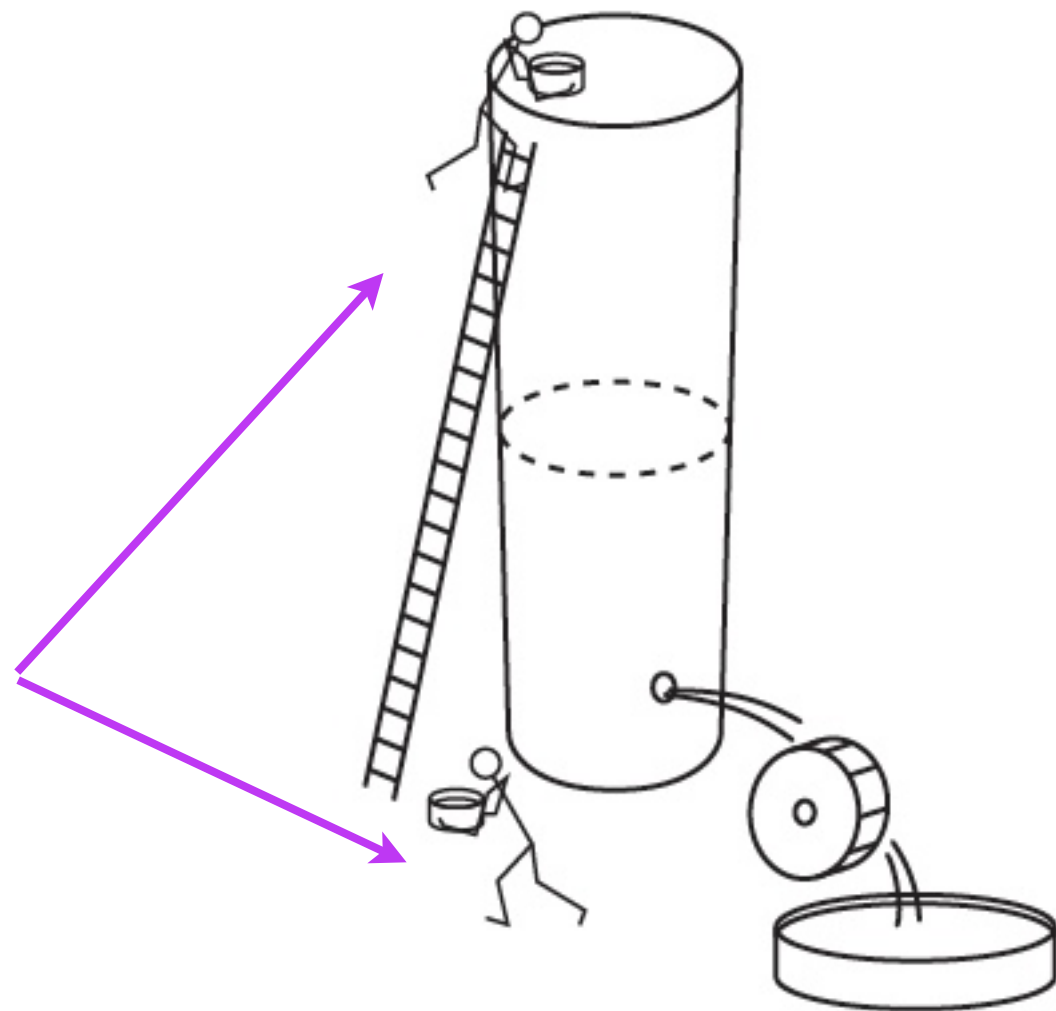


overview: the big three

VOLTAGE, RESISTANCE, AND CURRENT

Voltage

Electrical pressure or force (potential).
Measured in Volts.

The height of the water.

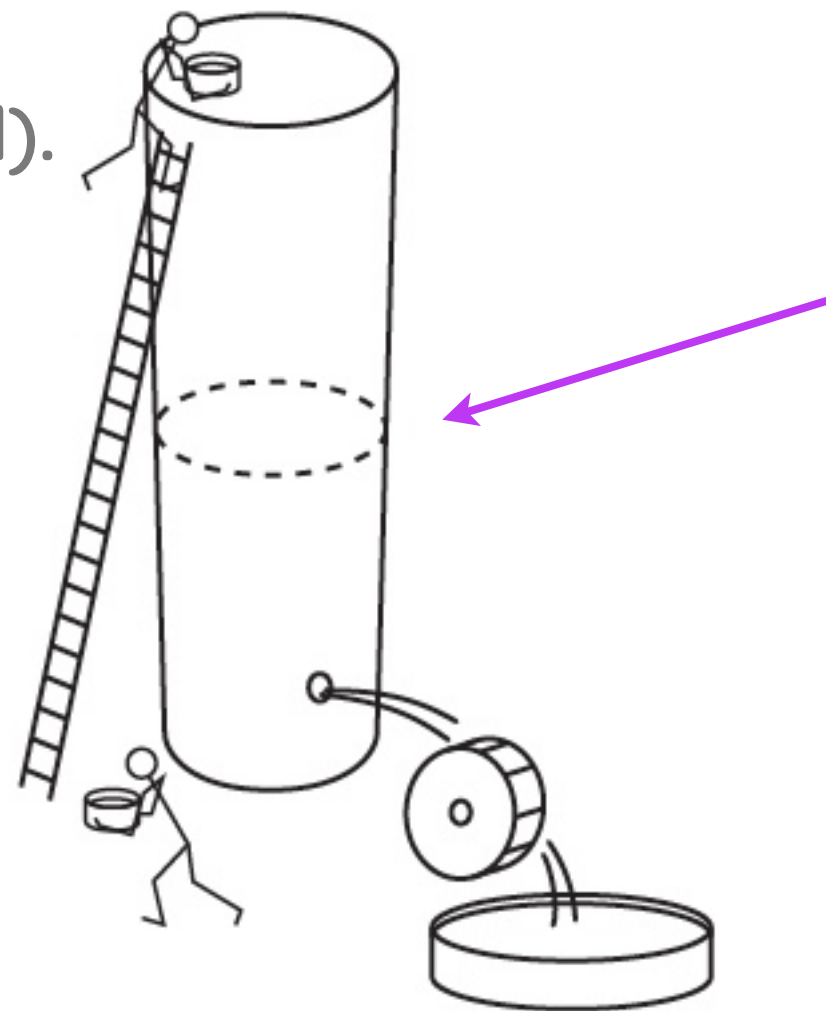

overview: the big three


VOLTAGE, RESISTANCE, AND CURRENT

Resistance

The amount that a conductor resists the flow of current.

It is measured in Ohms (Ω)

Size of the hole.

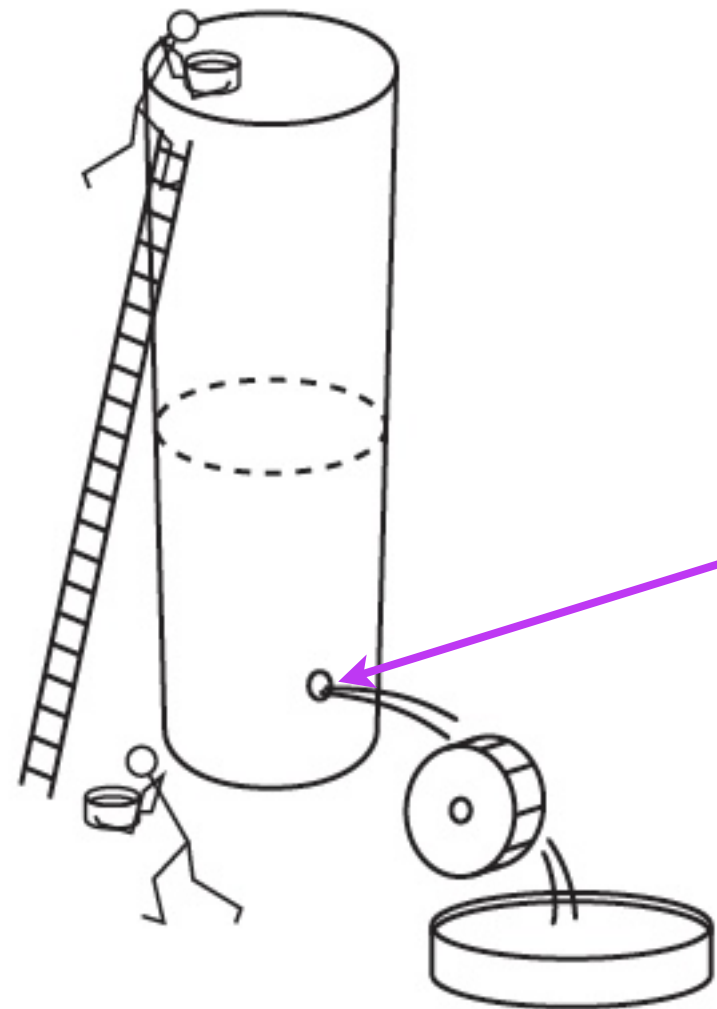

overview: the big three


VOLTAGE, RESISTANCE, AND CURRENT

Current

The quantity of electrons passing a given point in time.

Measured in Amperes (amps).

Volume of flow through the hole.

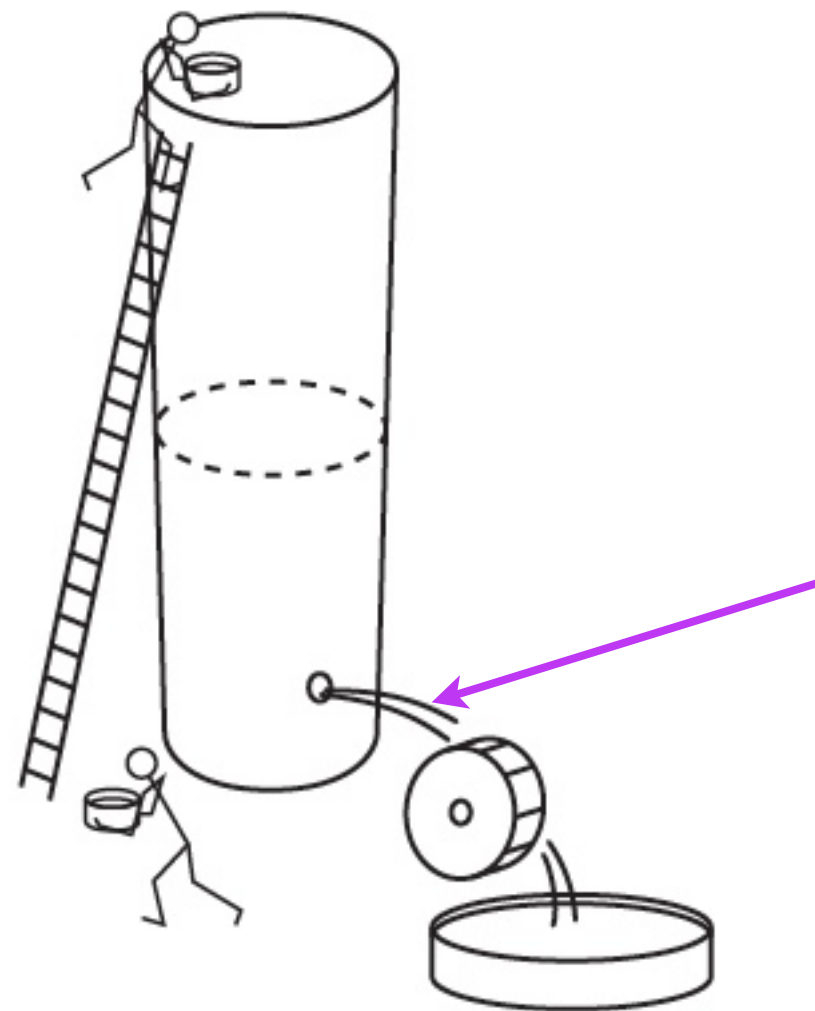


current

HOW DOES IT MOVE?

Current flows from an area of high charge (positive) to an area of low charge).

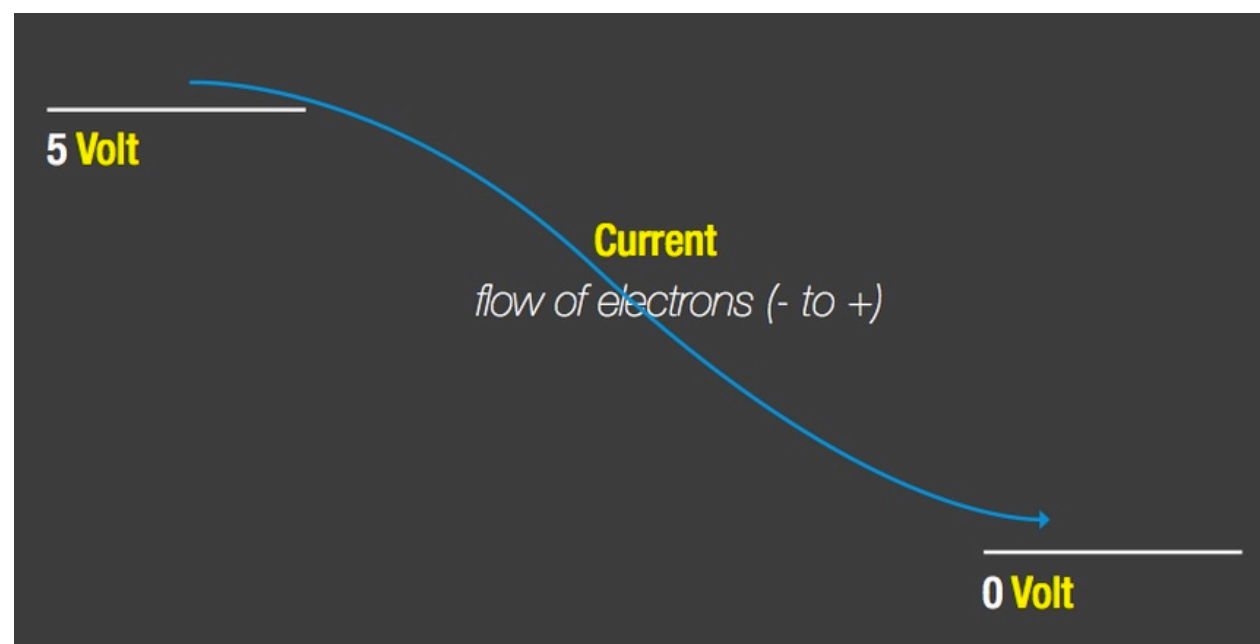But remember: *electrons* flow from negative to positive.



current

AC VS. DC (TO THE DEATH)

An electrical **current** can flow in either of two directions through a conductor.


current

AC VS. DC (TO THE DEATH)

An electrical **current** can flow in either of two directions through a conductor.

If it flows in only one direction (whether steadily or in pulses) it's called Direct Current (DC).

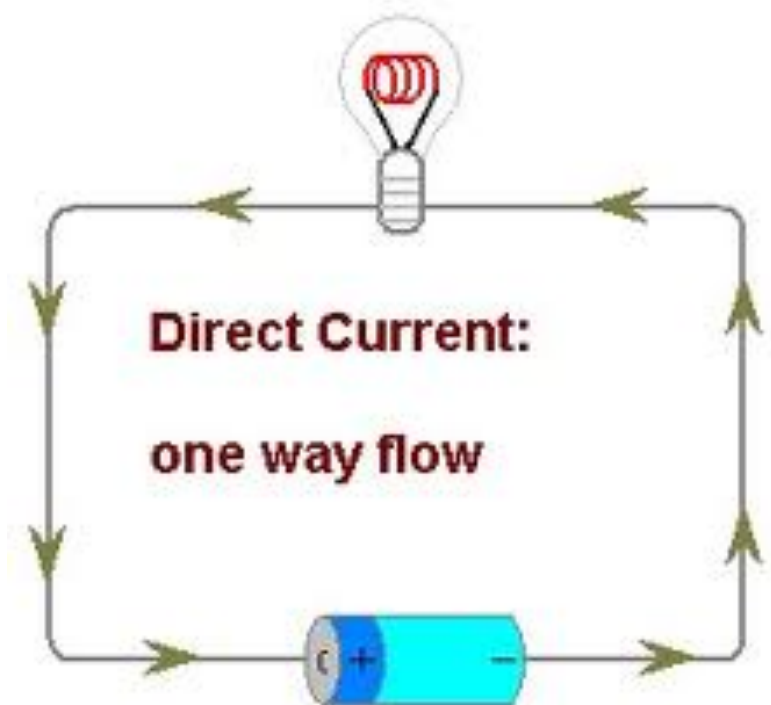This is the type of current you get from a battery (or from your computer).



current

AC VS. DC (TO THE DEATH)

An electrical **current** can flow in either of two directions through a conductor.

A current which alternates in direction or polarity is called Alternating Current (AC).

We will only be working with Direct Current.



resistance

YOUR ELECTRICAL BODYGUARD

A **resistor** limits the amount of electricity that can flow through a certain point.

If we didn't have these, we would fry our components.

We'll get into all the pretty colors in a sec.



voltage

HOW MUCH WORK CAN YOU DO?

Voltage is the potential for doing work. The more voltage you have, the more you are capable of putting in long hours.

If we didn't have these, we would fry our components.

We'll get into all the pretty colors in a sec.



another analogy

THE CAFFINATED DT-ER

Voltage is the potential for doing work. The more voltage you have, the more you are capable of putting in long hours.

Perhaps another analogy is appropriate...

Caffeine in DT.

Without it, you might do this...



ohm's law

THEY ARE ALL RELATED!

Given any of two the previous, you can find the remaining two by using **Ohm's law**.

$$V = I \times R$$

$$I = V/R$$

$$R = V/I$$

V = difference in voltage between two points in a simple circuit

R = the resistance in ohms between the same two points

I = the current in amps flowing through the circuit between the two points.

ohm's law

THEY ARE ALL RELATED!

Why would you need this?

Because we are going to start building circuits!




circuits

MUCH SIMPLER THAN IT SOUNDS.

A **circuit** is a path that electrical current flows through. Circuits are made from conductive material. Electricity can flow through any material that is conductive.

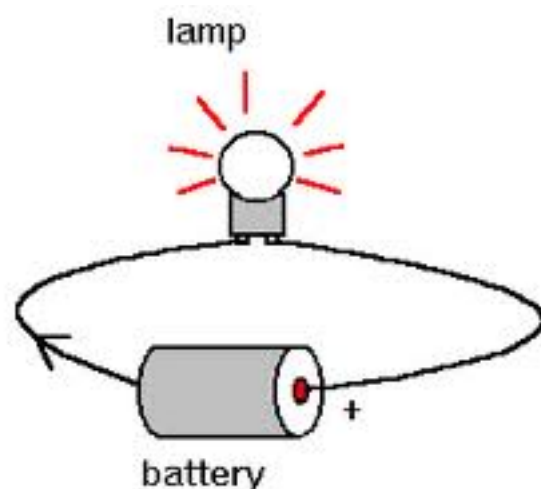A circuit can be as simple as a battery connected to a lamp or as complicated as a digital computer.



conductors

LET IT FLOW

A material where the electrons are free to move around and create electric currents.

Examples: copper, aluminum, silver, steel, gold, etc.
Keep in mind different conductors have different levels of resistance.



insulators

NOT SO MUCH FLOW

Insulators have the opposite effect on electrons. Electrons are not able to easily move around within insulators.

Examples: glass, plastic, rubber, air, wood




resistors

COLOR-CODED

Resistors have an interesting coding system.

Become well-acquainted with it.

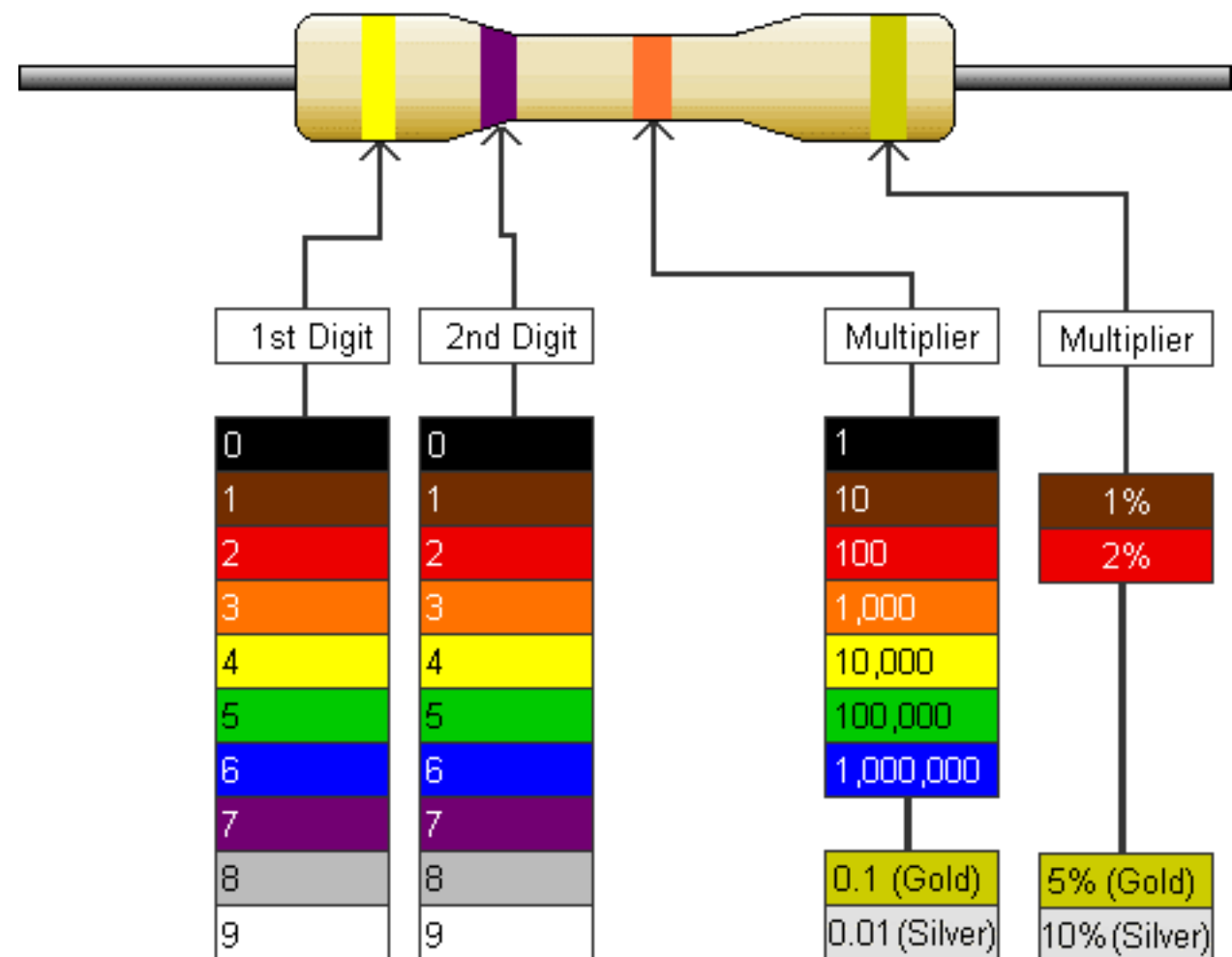


resistors

COLOR-CODED



What are the values?

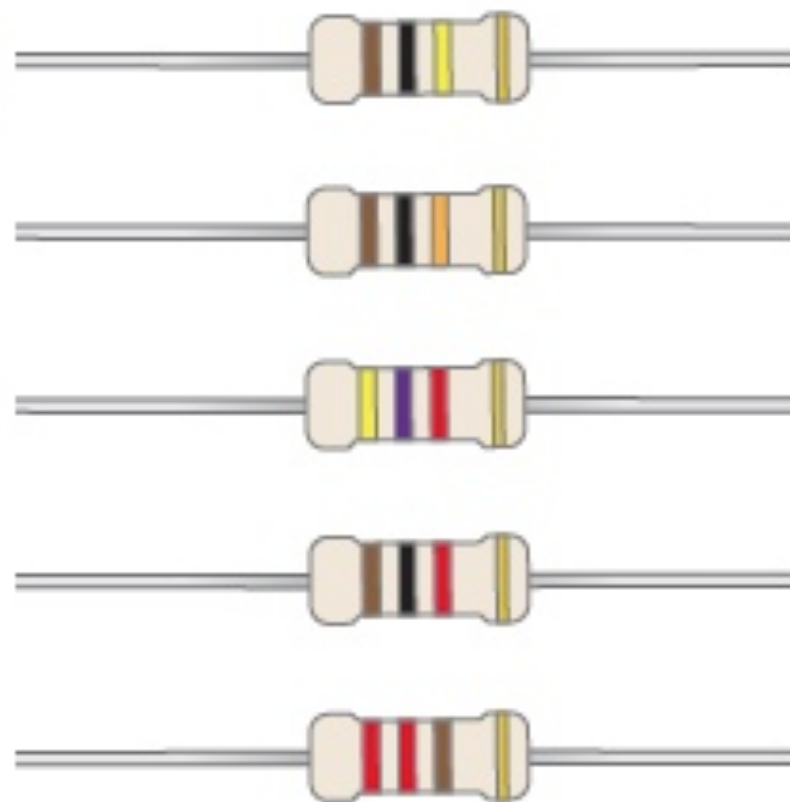


resistors

COLOR-CODED




They are actually quite common...

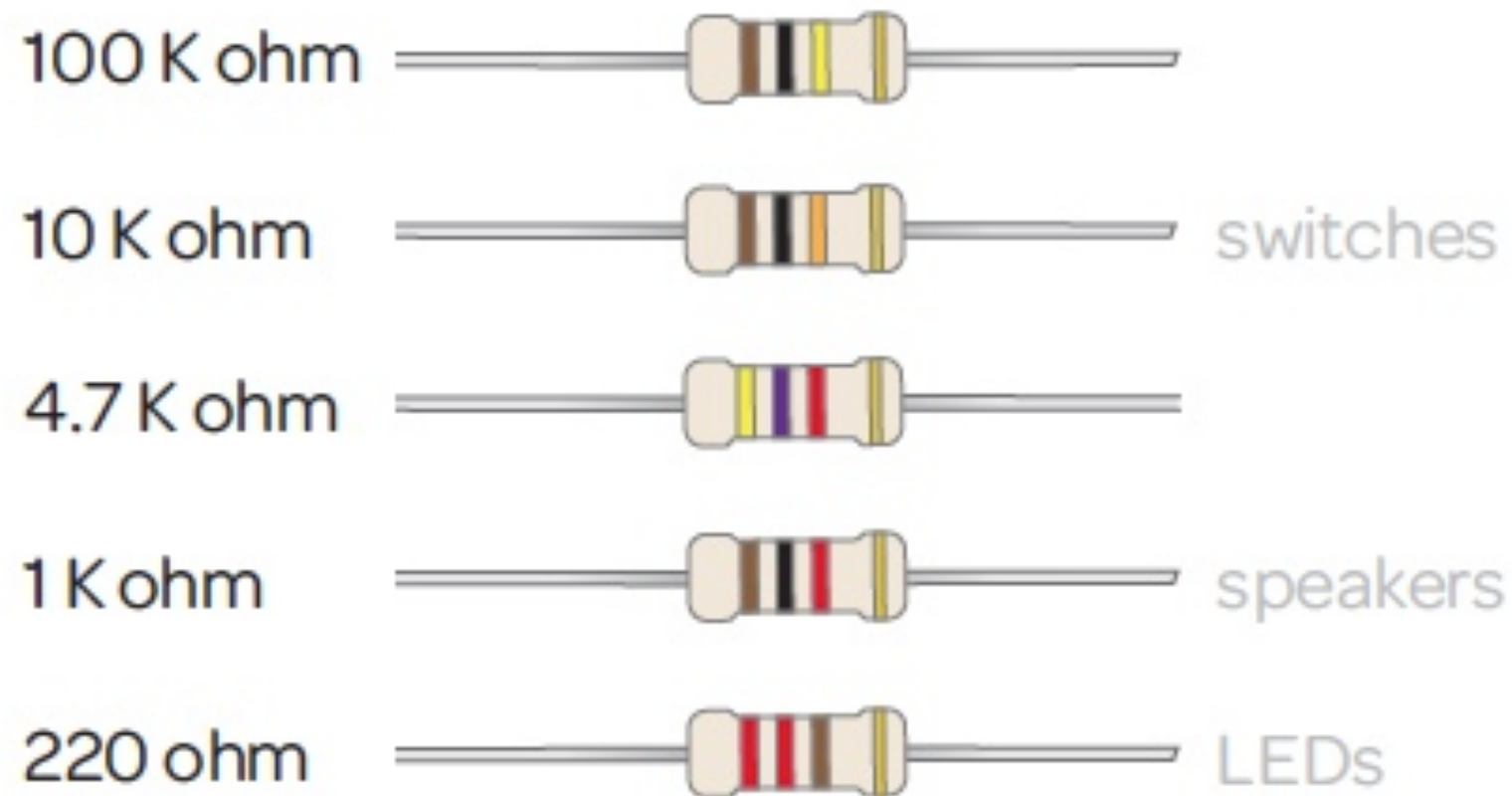


diodes

ONE WAY STREET

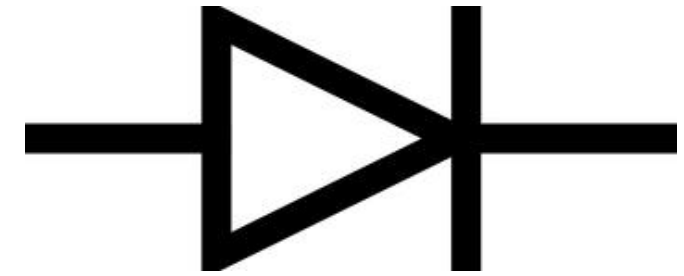

An electronic component made up of a semi-conductive chip, which only conducts electricity in one direction.

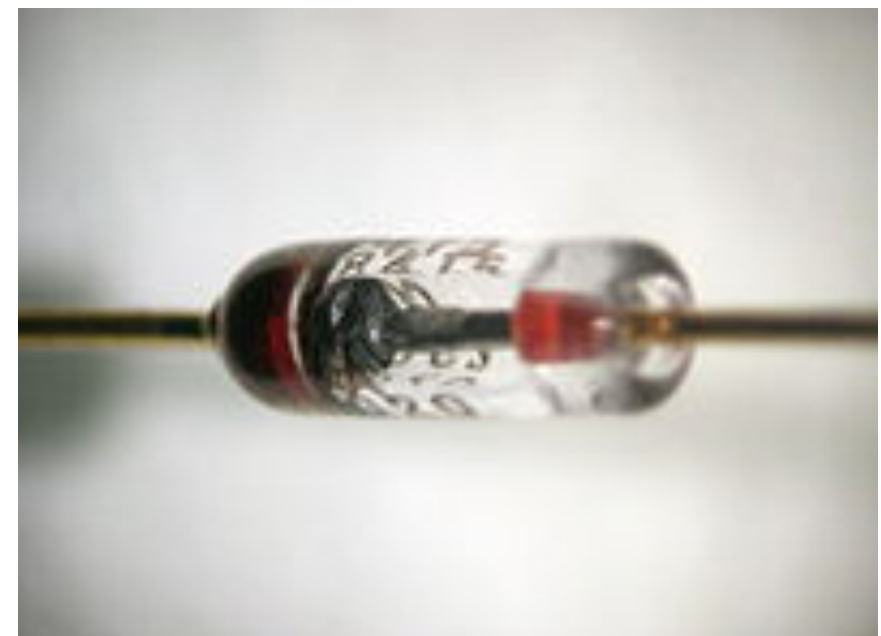We'll only be dealing with one type of diode:
Light Emitting Diodes




LEDs

PRETTY



LEDs


THE SPECIAL DIODES

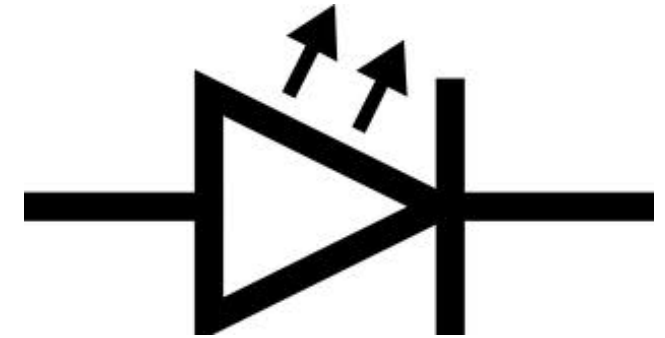

All diodes emit some electromagnetic radiation when forward biased.


Diodes made from certain semiconductors (like gallium arsenide phosphide) emit considerably more radiation than silicone diodes.

= They Light UP!

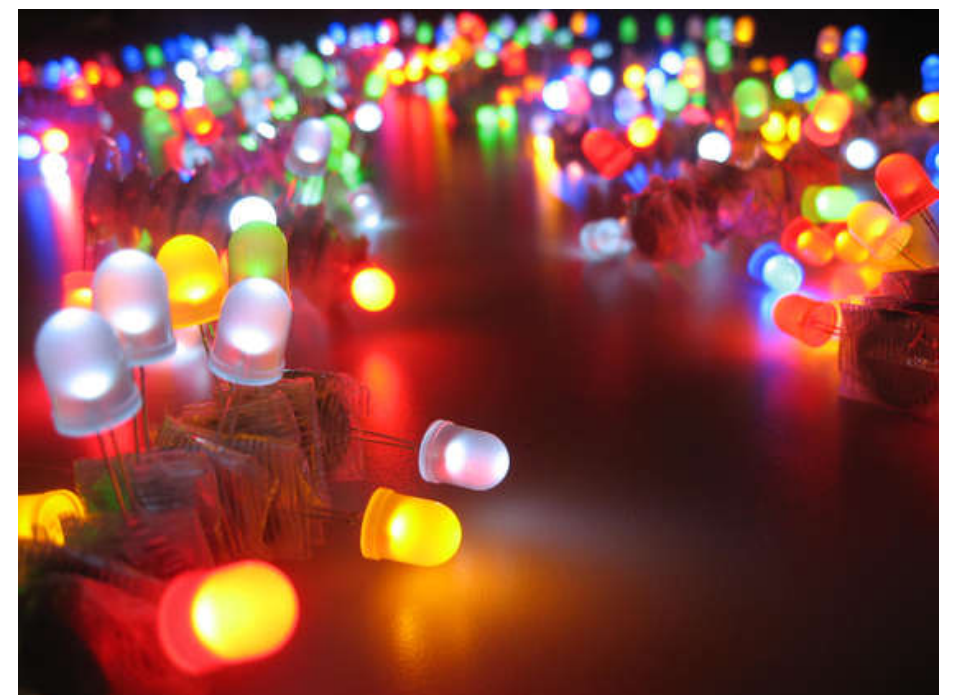

LEDs

THE SPECIAL DIODES

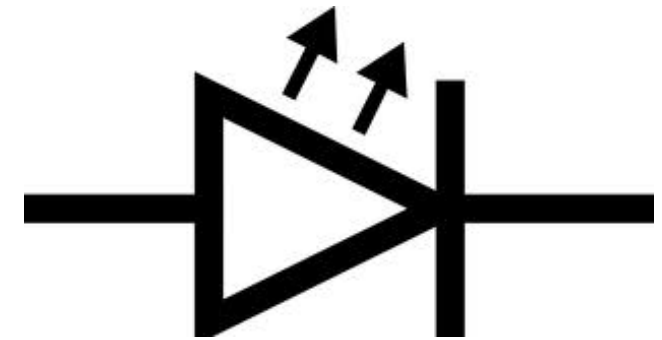

CATHODE

ANODE

ground

power

-

+

breadboard

BREAK IT TO MAKE IT

A **prototype board** for putting together circuits.


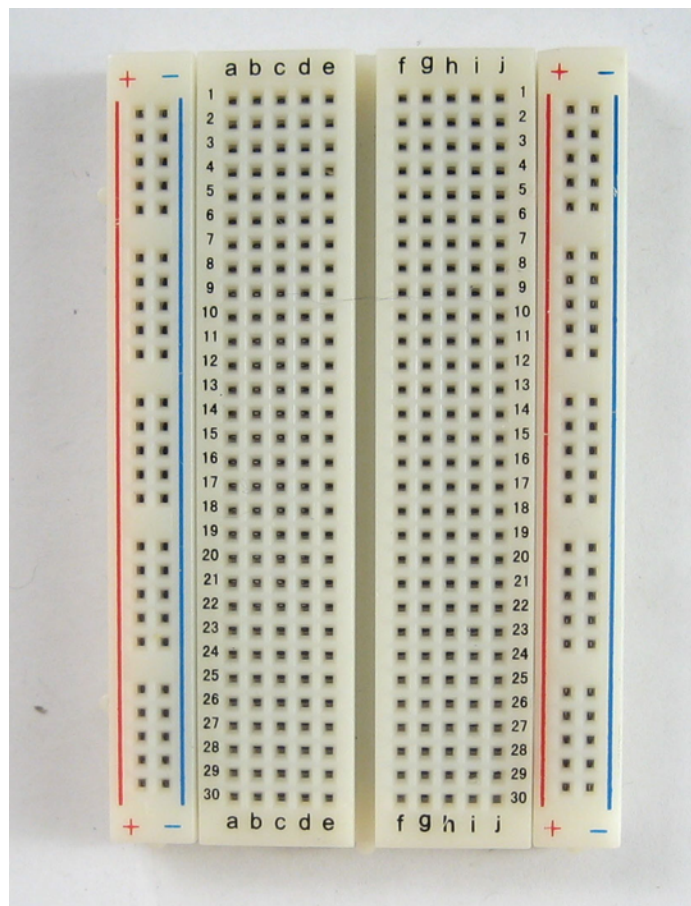


Figure 1. Pin Diagram of a Solderless Breadboard

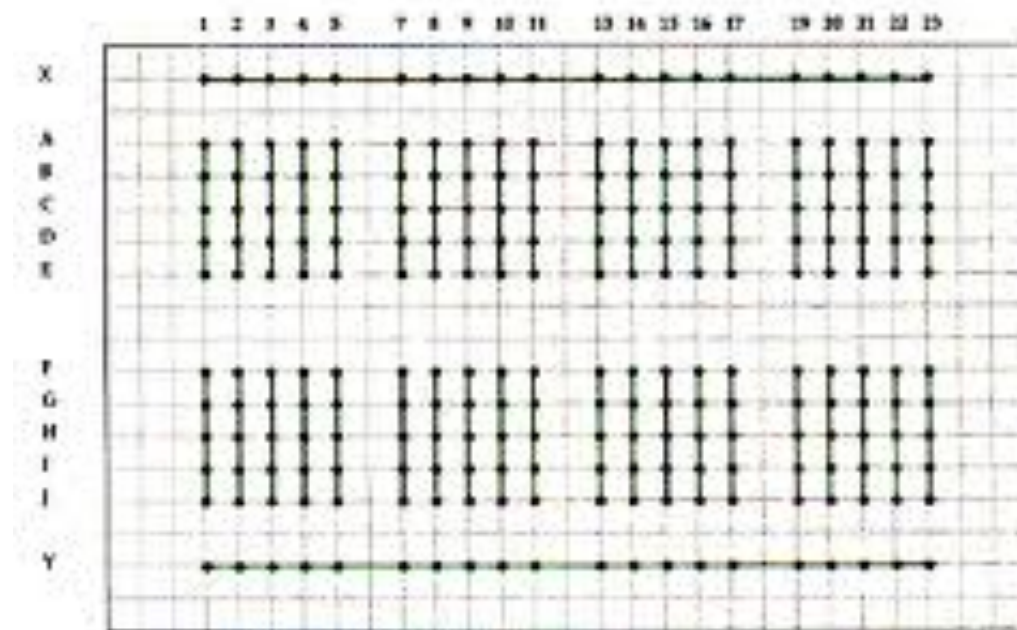


Top view of a solderless breadboard. Colored lines indicate internal connections. Dots mark plug points.

make light!

BE PROMETHEAN

Make an LED light up.

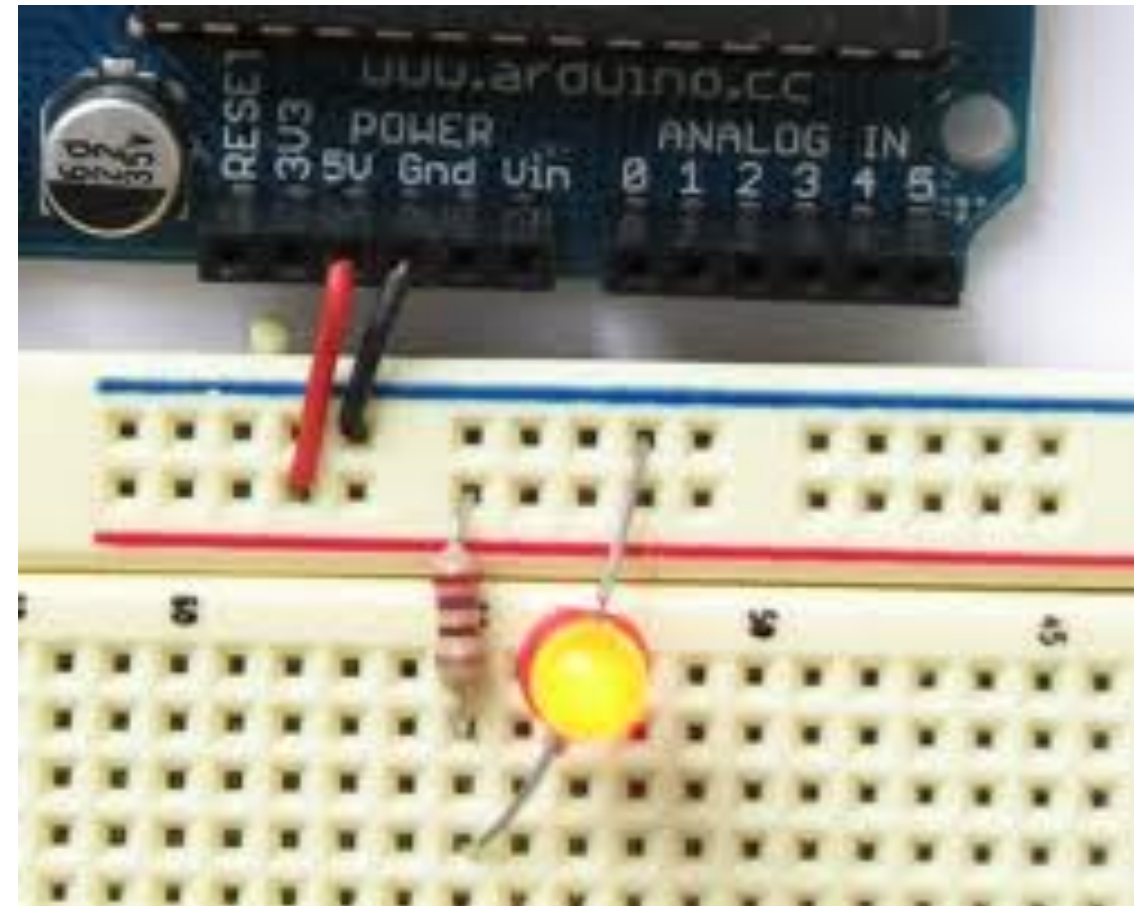

field trip


TO THE PCOMP ROOM!

Soooo many resources...so little time.

make light!


BE PROMETHEAN

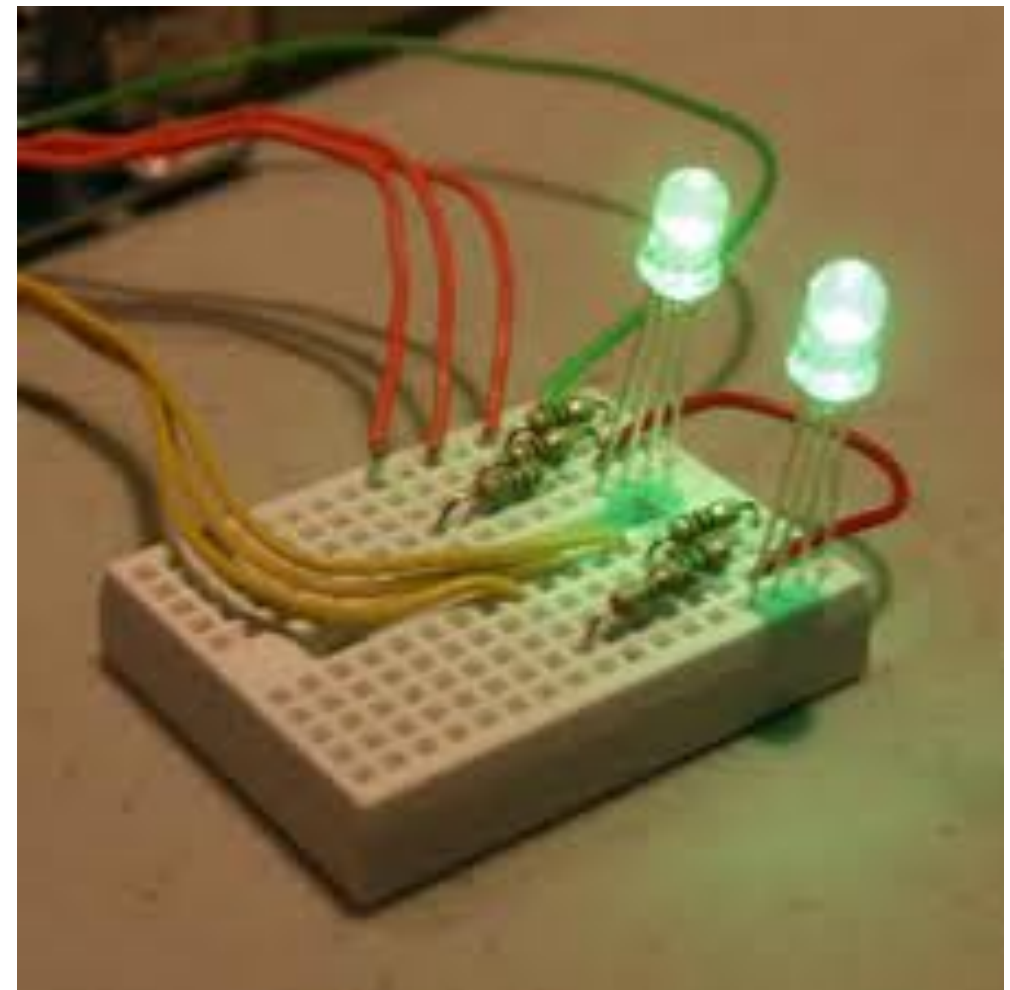But **two** LEDs are
always better than
one...




switch


BREAK IT TO MAKE IT

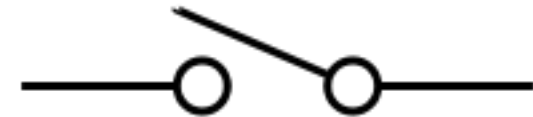

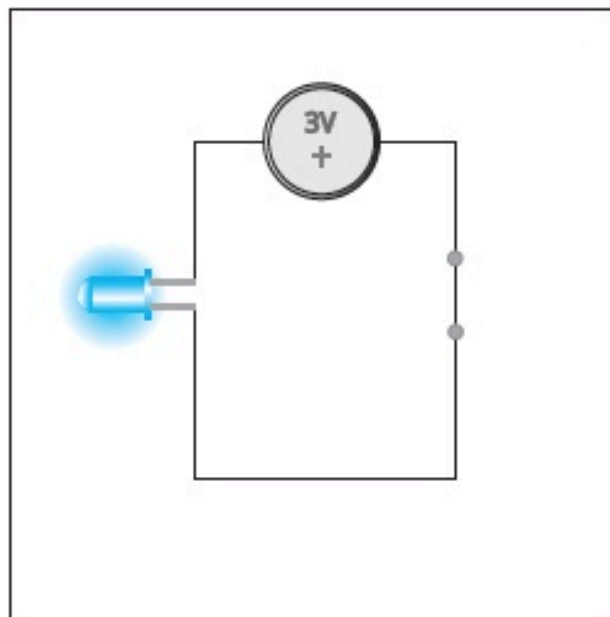
A **break** in the circuit that can be opened or closed.



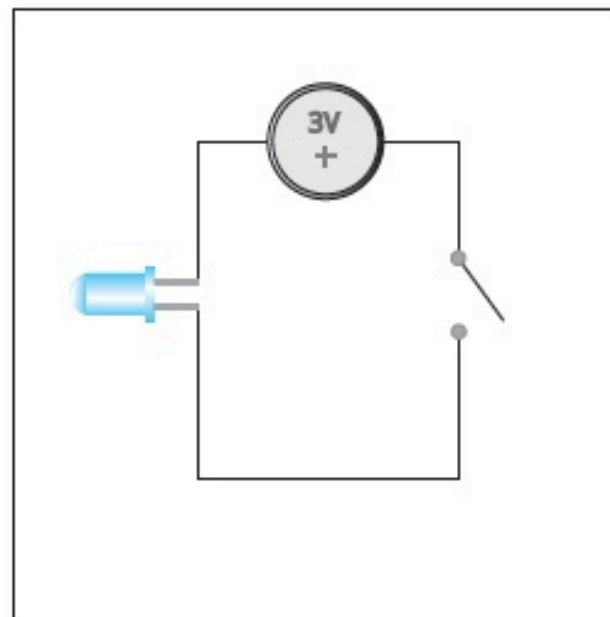The circuit is **CLOSED** so the LED is **ON**.



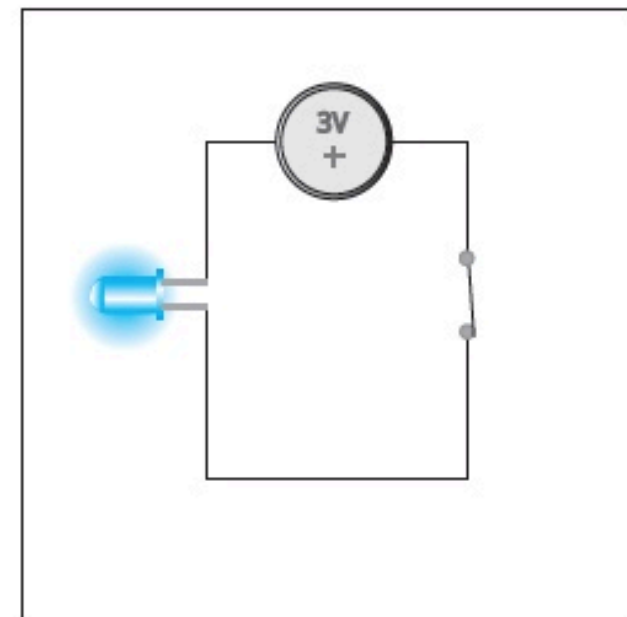The circuit is **OPEN** so the LED is **OFF**.





The circuit is **CLOSED** so the LED is **ON**.

parallel circuits

MORE THAN ONE WAY TO WIRE

You can wire more than one LED in parallel or series.

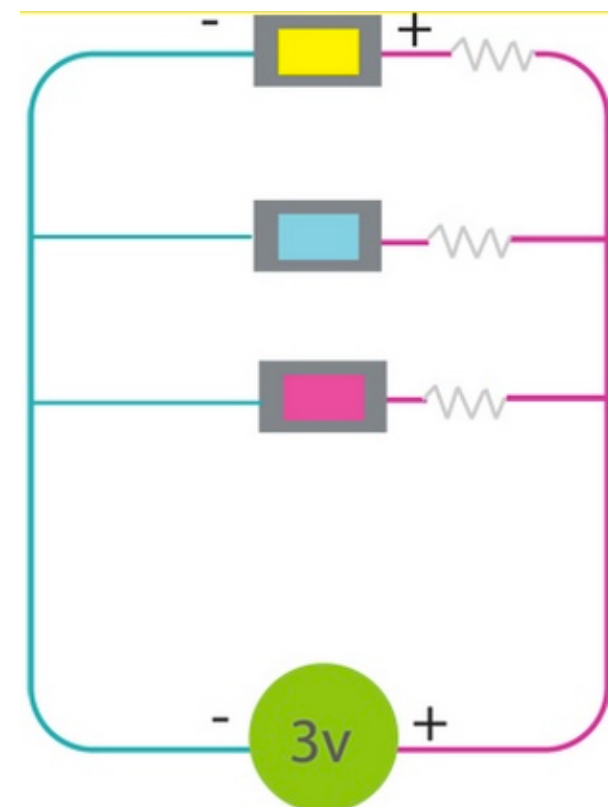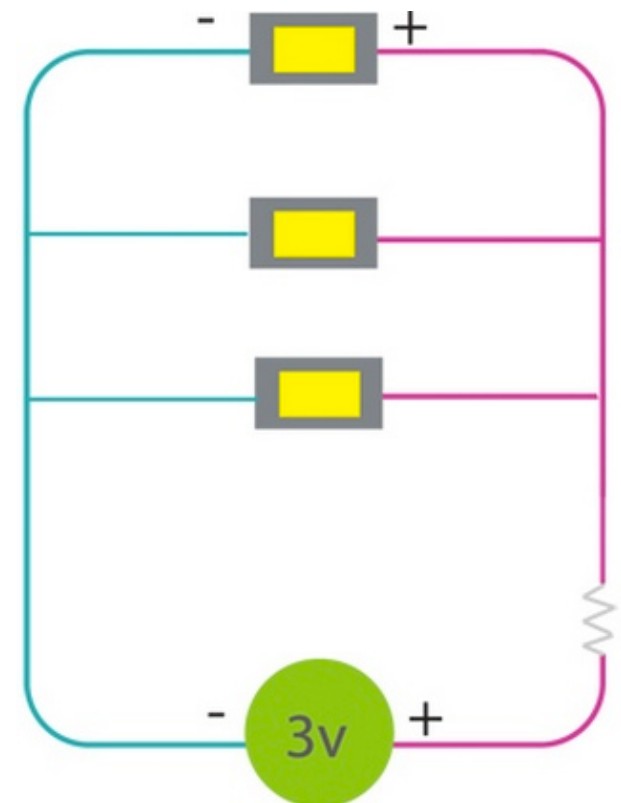Parallel circuits share the same **VOLTAGE**.




series circuits

MORE THAN ONE WAY TO WIRE


You can wire more than one LED in parallel or series.

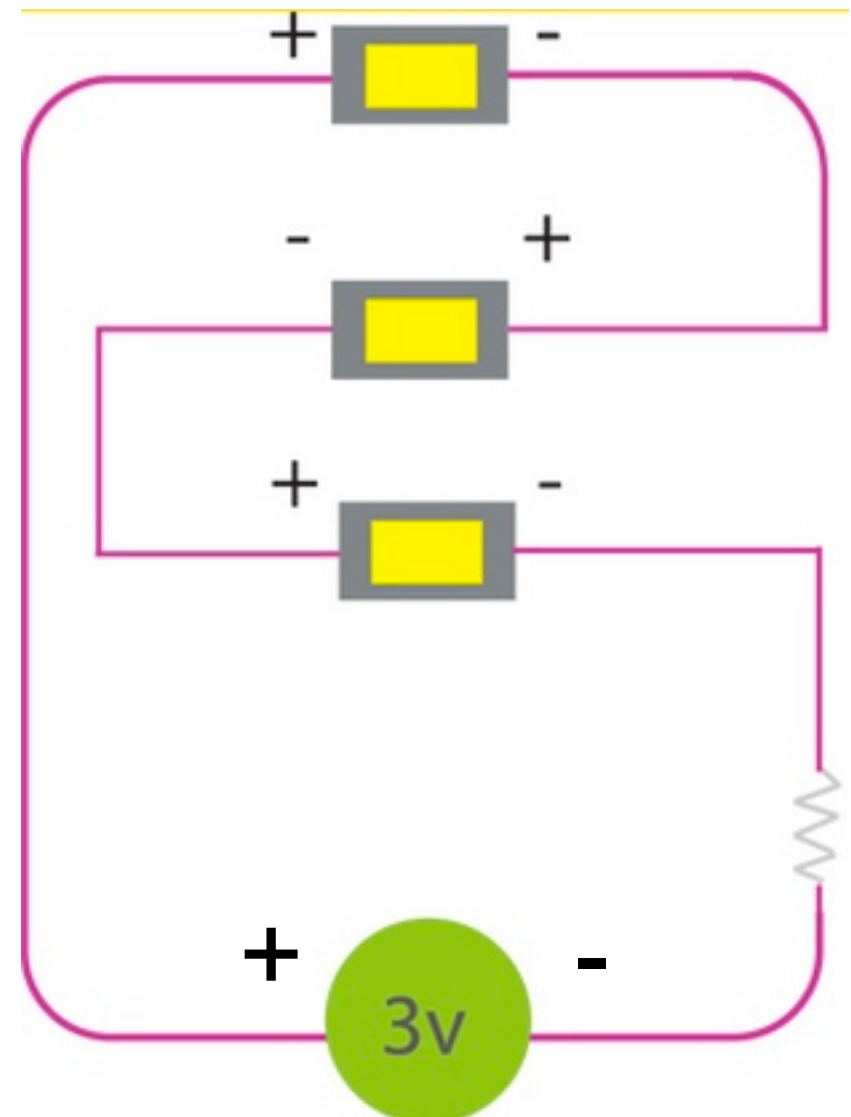Series circuits share the same **CURRENT**.




switch


BREAK IT TO MAKE IT

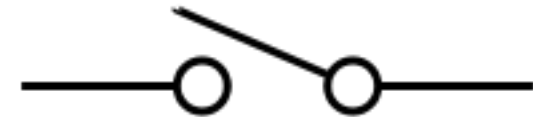

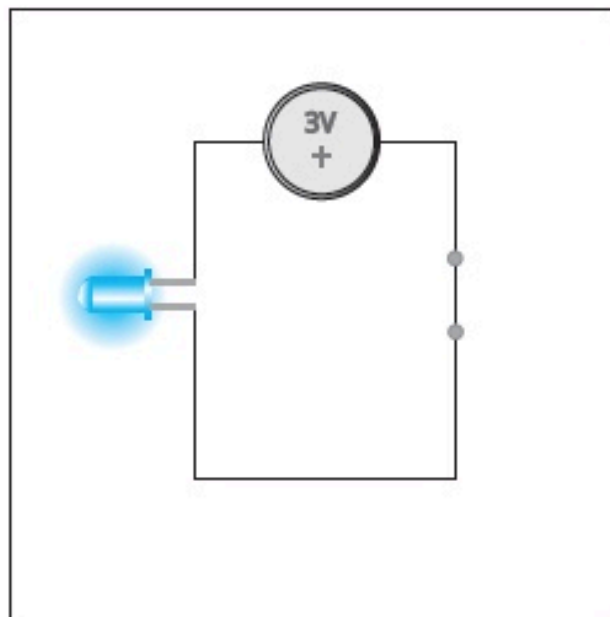
A **break** in the circuit that can be opened or closed.



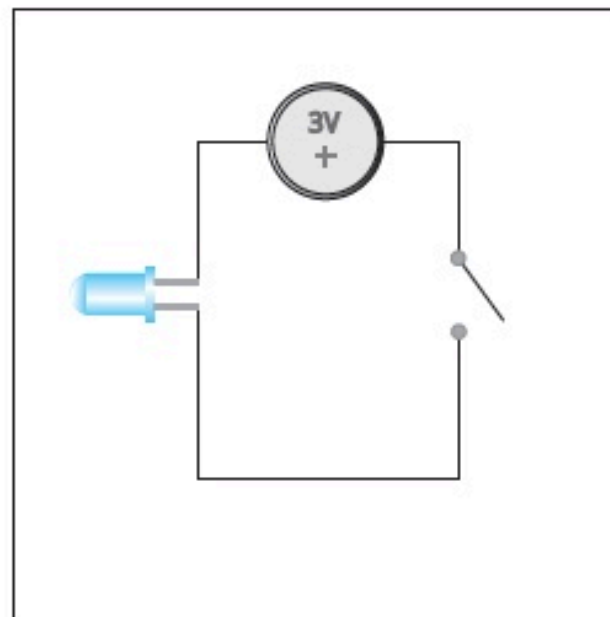The circuit is **CLOSED** so the LED is **ON**.



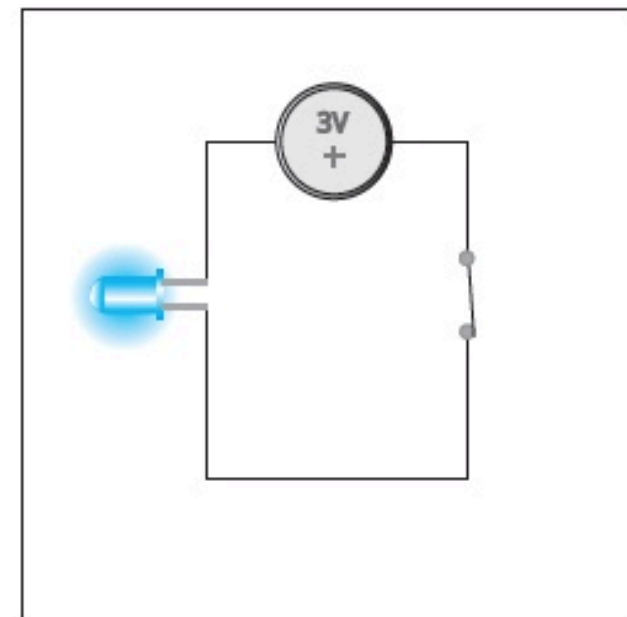The circuit is **OPEN** so the LED is **OFF**.



The circuit is **CLOSED** so the LED is **ON**.